

A Micro-Power CMOS RF Front-end for Embedded Wireless Devices


**R.Rofougaran, T. H. Lin, F.Newberg, W. J. Kaiser
UCLA Electrical Engineering**

Outline

- **Introduction to Wireless Integrated Network Sensors (WINS) Project:**
Network, Applications, Nodes
- **Unique Front-end Requirements**
- **RF Architecture:** Preselector, LNA and Mixer Architecture
- **Future work:** (WINS integration)
- **Summary**

(Wireless Integrated Network Sensors) WINS

- Low-Power Networking

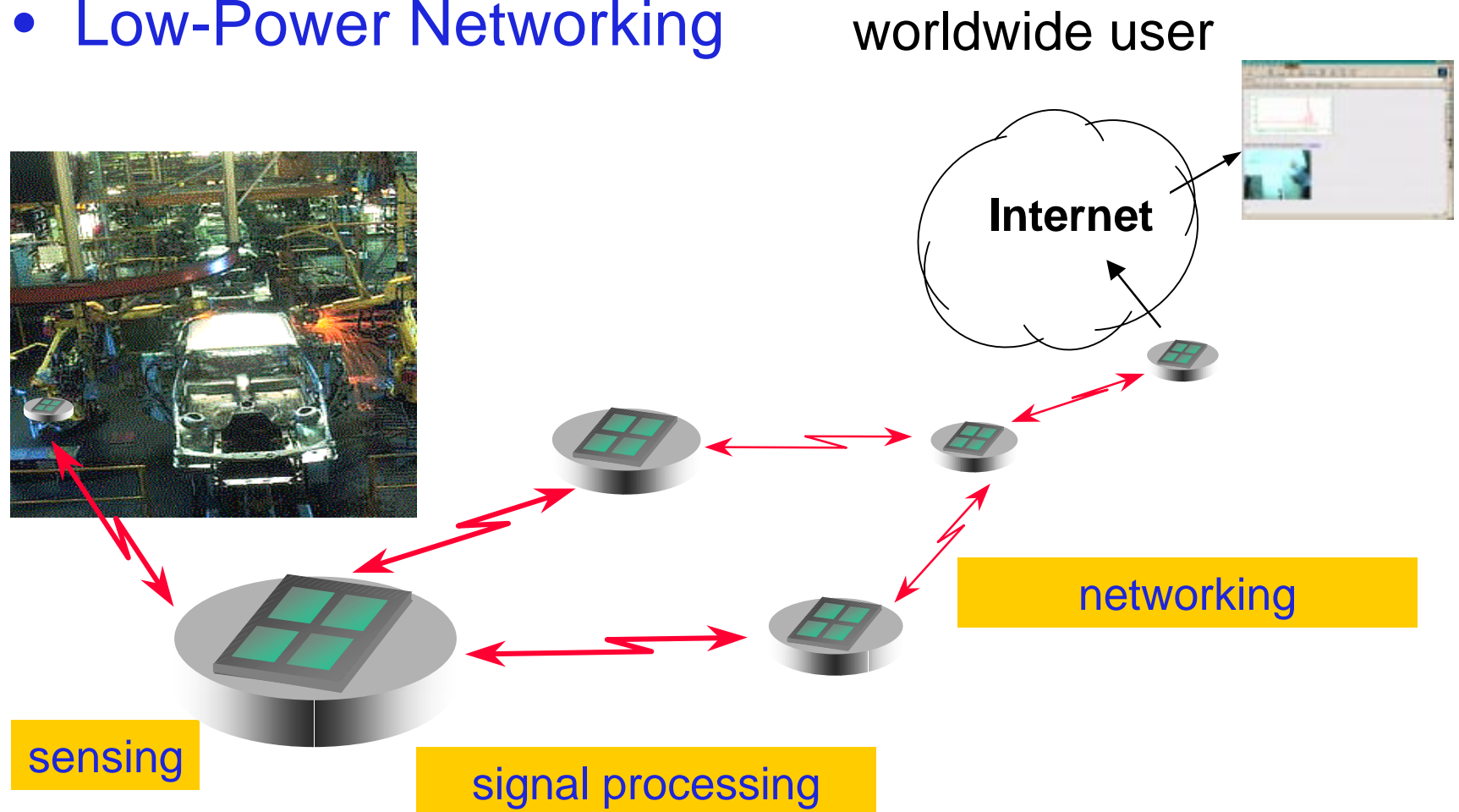

WINS Applications



Consumer



Transportation systems



Defense security



Medical instrument internetworking



Industrial controls

Network Characteristics

- Dense node distribution
- Short range (< 30m)
- Low bit rate (< 100kbps)
(Typical sensor systems are band limited)
- Latency tolerant
- Compact cell
- 3 year life
- 100 μ W average
- 3 mW peak


Implement multihop for power:

RF path loss:




$$P_{\text{rec}} \propto 1/R^\alpha \quad (\alpha \approx 3 - 5)$$

Relative system power advantage for
N-hop chain:
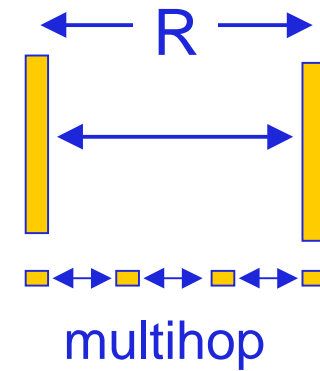
$$P_{\text{tot}}(N)/P_{\text{tot}}(1) \propto 1/N^{(\alpha-1)}$$



WINS Nodes

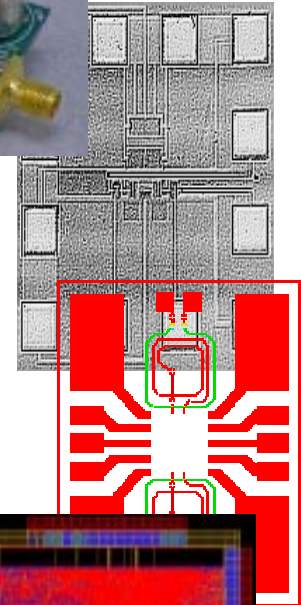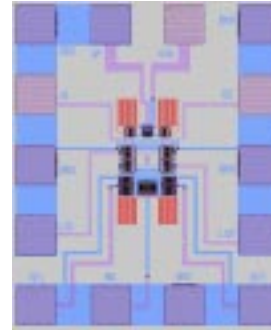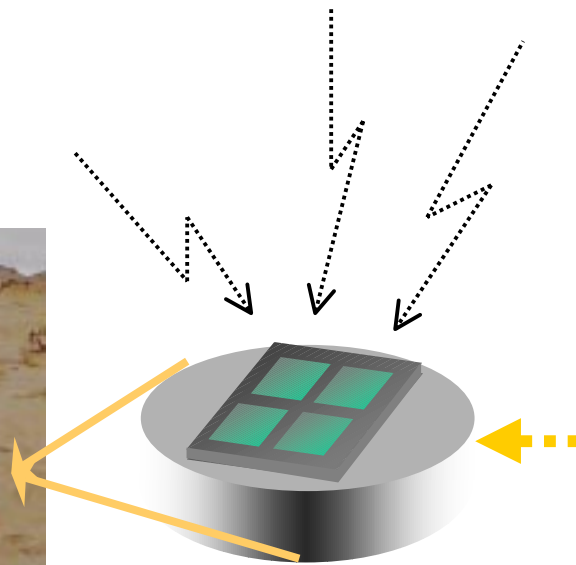

- WINS RF Modem
- Network Interface
- Memory
- Microcontroller
- State Machine
- DSP
- ADC
- Sensor Interface
- Sensors



WINS vs. Existing wireless system

Characteristic	Wireless LAN	Cellular Telephony	WINS
Range	~ 200m	~ 5km	$\leq 30\text{m}$
Data Throughput	~ 2-10Mbps	~ 10kbps	$\leq 100\text{kbps}$

- Conclusions:
- Range and bandwidth reduction : ***60 - 80dB gain in link budget***


Why Design a New Receiver?

- **Performance Specifications of receivers:**

	Cellular	Bluetooth	WINS
Noise Figure	8dB	Est (- 26)	~ 25dB
Sensitivity	-102dBm	-70dBm	~ -70dBm
Data rate	~10 kbps	1Mbps	≤ 100kbps
Current consumption	35 - 40mA	≤ 20mA	~ 1 mA

- **Challenge:** Minimum noise figure and best sensitivity for long range communications.
- **Specifications of the front-end receiver for WINS project:**
 - Digital CMOS transistor
 - Current consumption ≤ 200 μ A
 - Gain \cong 20 - 25dB
 - Noise figure \cong 20 dB
- **Challenge:** Micro power for short range communications (30 m)


Receiver Architecture

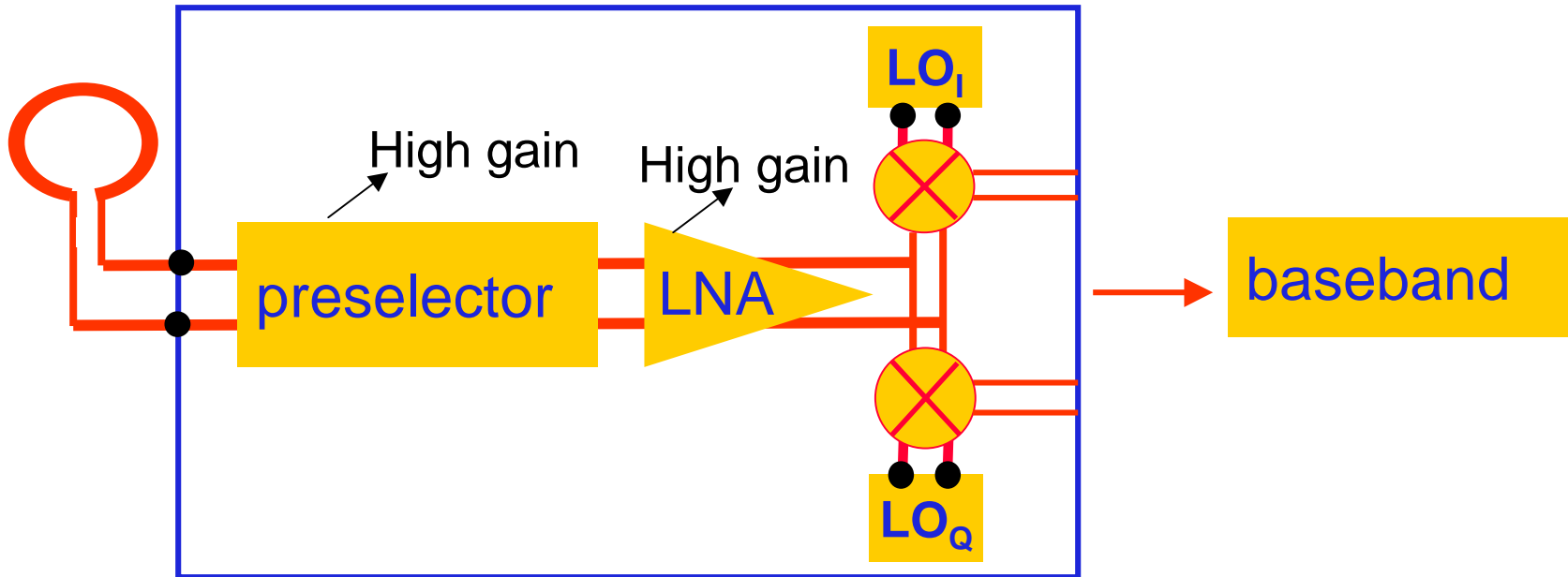

Goal: 1mA entire receiver system peak current drain

- High-Q inductive loads
- Off chip integration: LTCC components


Differential Preselector/LNA

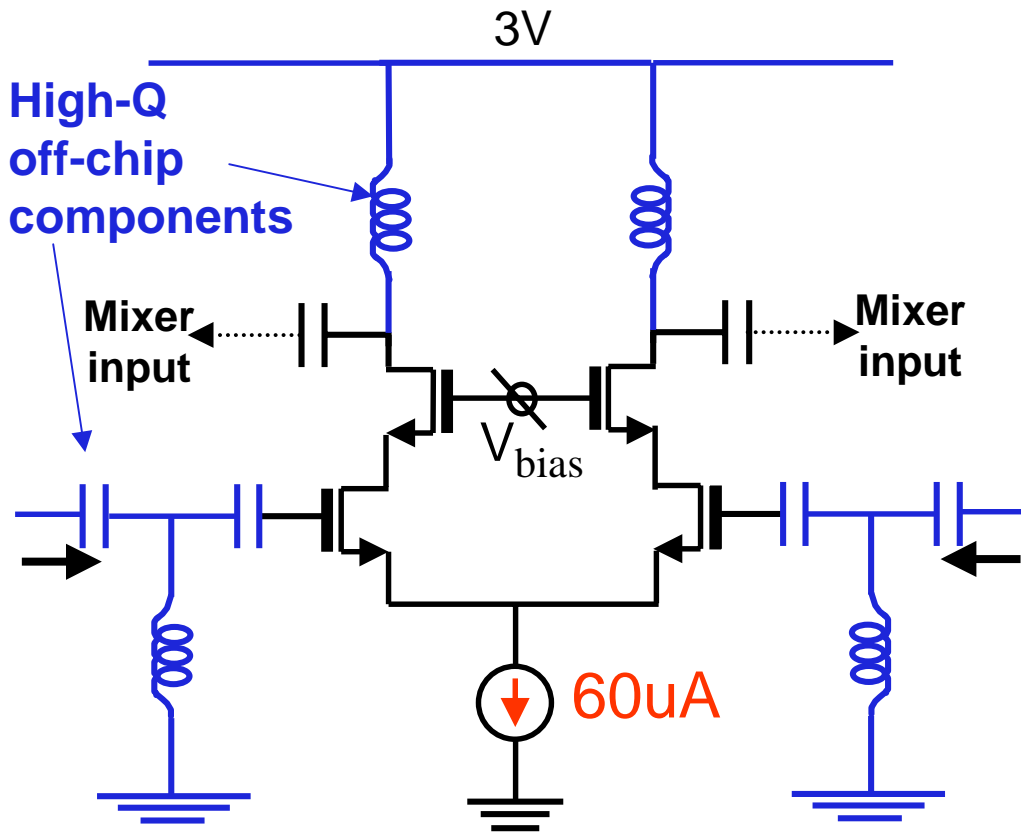

Gain achieved by:

- **Preselector:** High Q elements
- **LNA transistors g_m :** Small due to the small current and relatively small transistor sizes
- **LNA output Impedance:** High Q components to generate large impedance at the output
- **Mixer input:** High impedance

Preselector

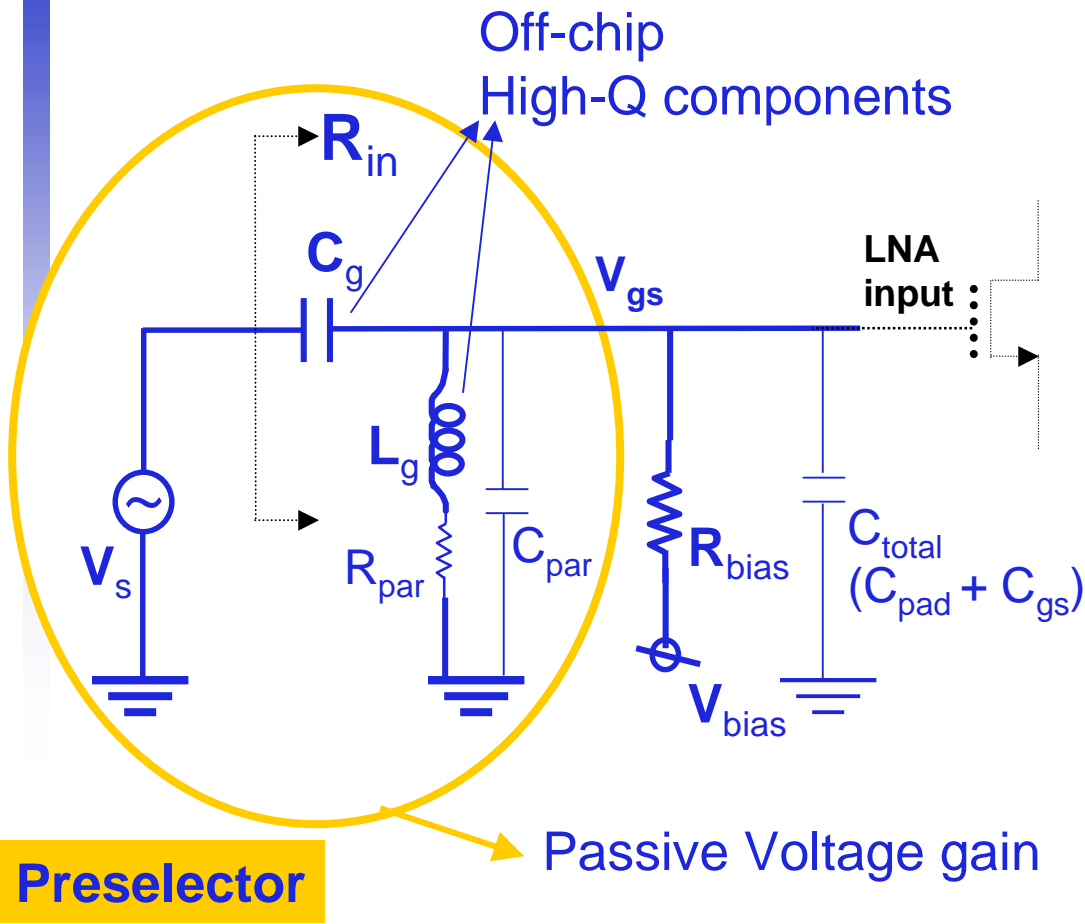

- Filtering
- Matching

Choose L and C:

$$\omega_{res} = R / \sqrt{L((C_g + C_{total}) R^2 - L)}$$

$$R \rightarrow \infty \quad \omega_{res} \approx 1 / \sqrt{L(C_g + C_{total})}$$


Input impedance at ω_{res} :

$$R_{in} \approx L / R_{bias} (C_g || C_{total})$$

- Gain from V_s to V_{gs} :

$$V_{gs} / V_s \approx R \sqrt{(C_g || C_{total}) / L}$$

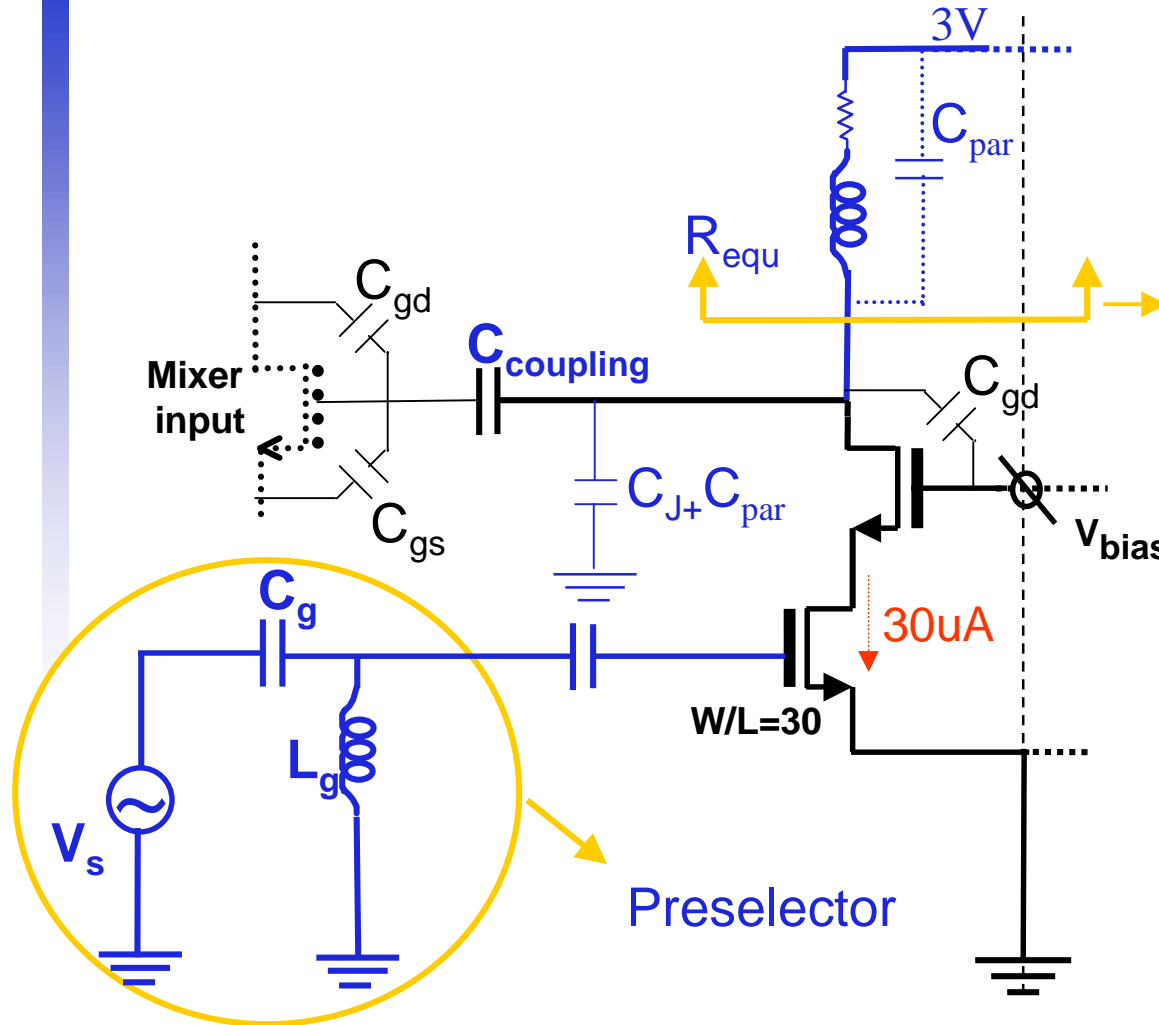Half Circuit of the Preselector/LNA Including Off-chip Elements



- LNA output impedance at ω_{res} :


$$R_{\text{equ}} = L / RC_{\text{total}}$$

- Total gain:

$$A_v = g_m R_{\text{equ}} A_{\text{preselector}}$$


Mixer

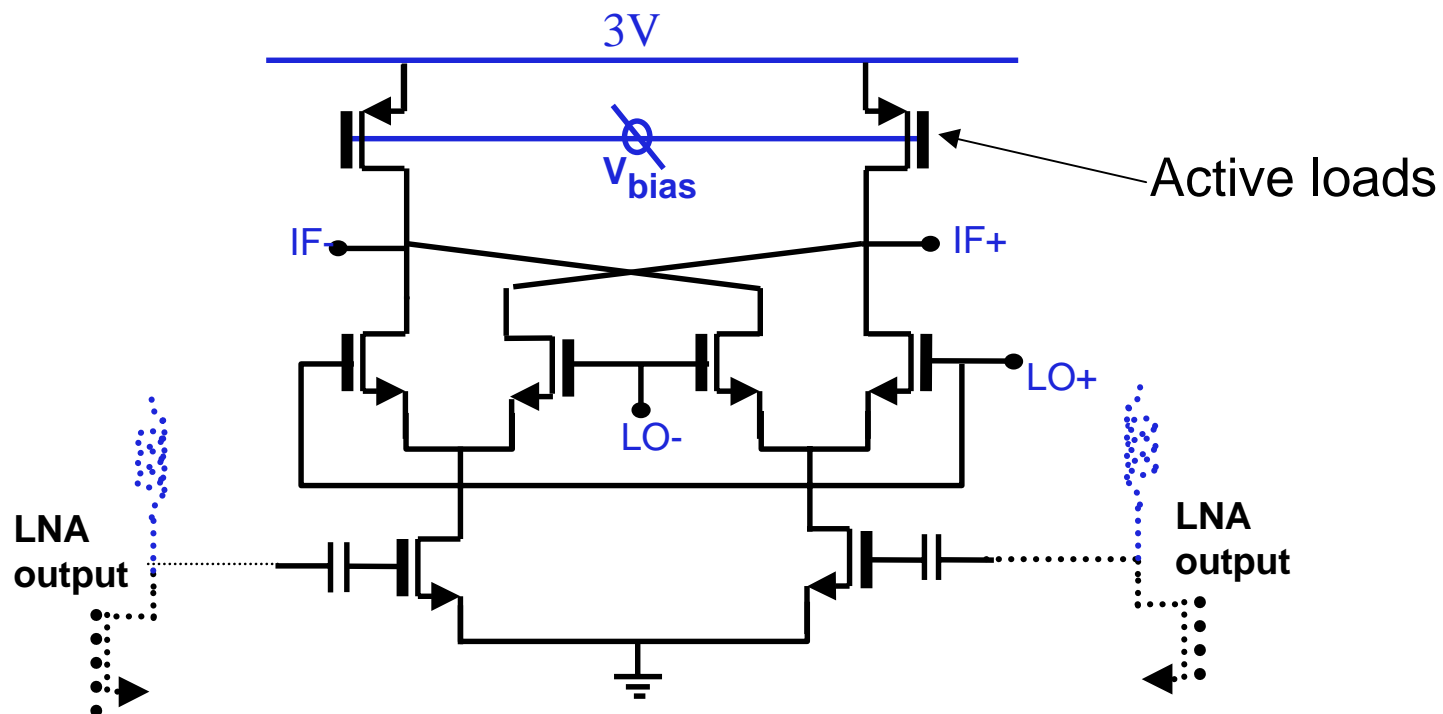- Weak inversion
- Double-balanced Gilbert Cell
- Direct conversion
- 50 μA core supply current at 3V
- Output bandwidth $> 100\text{kHz}$
- High output impedance




Test Setup


- Testing Preselector, LNA and Mixer:

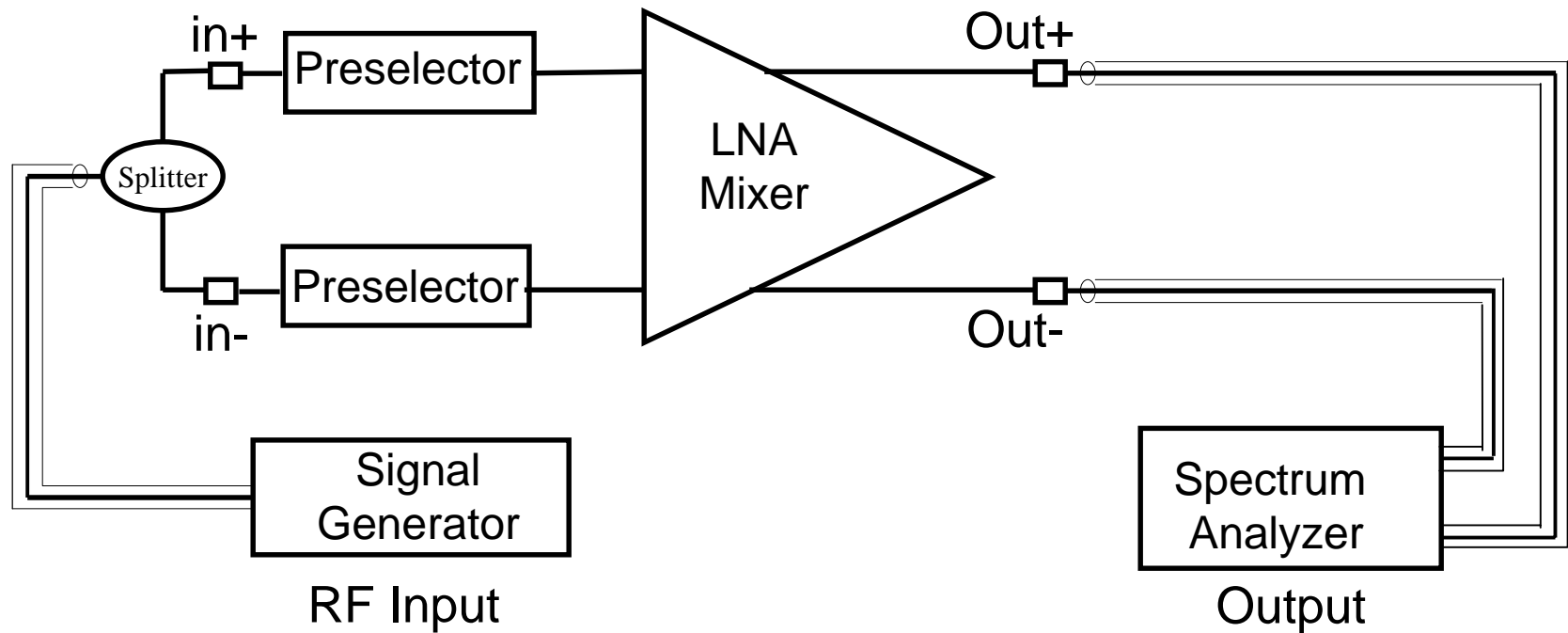

Testing

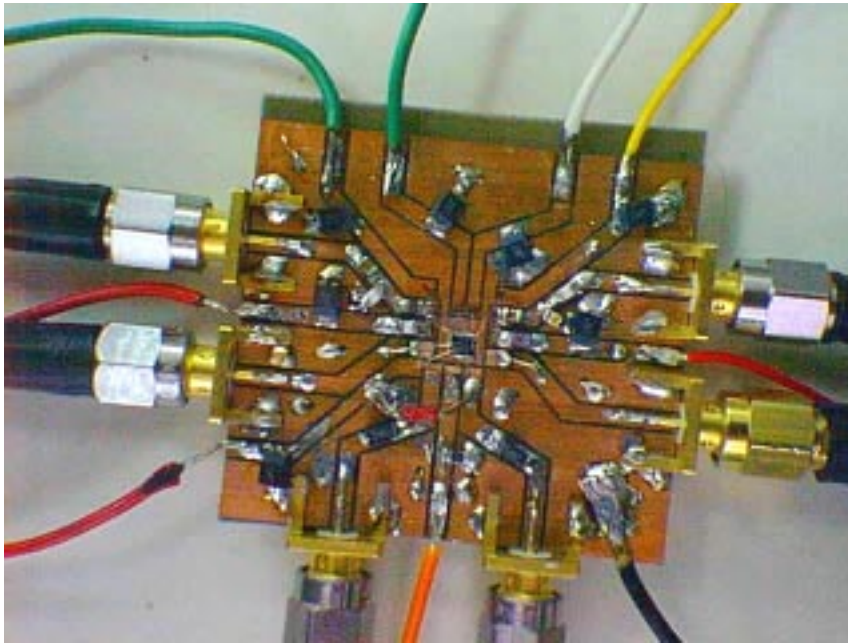


Front-end with off-chip components

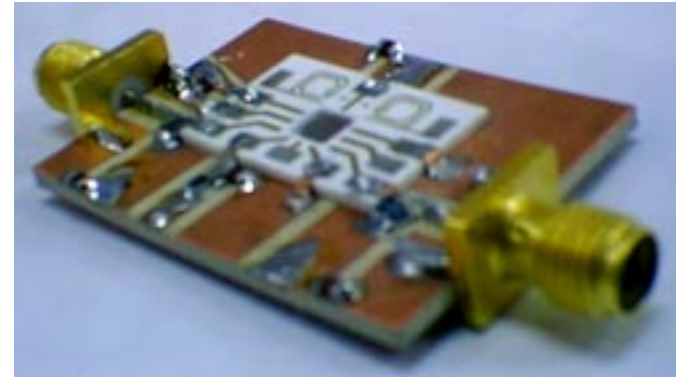


VCO on LTCC substrate

Gain Results

Gain = 25dB

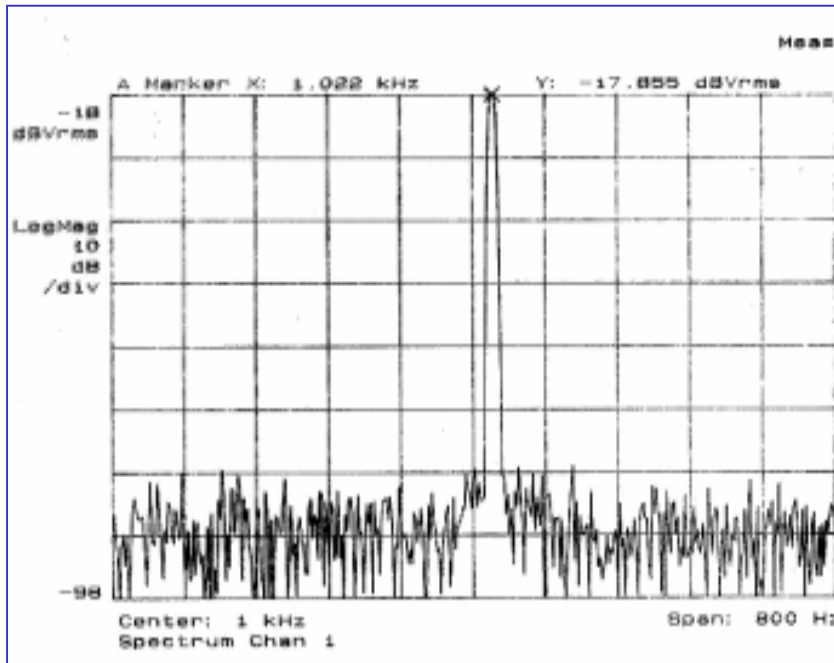


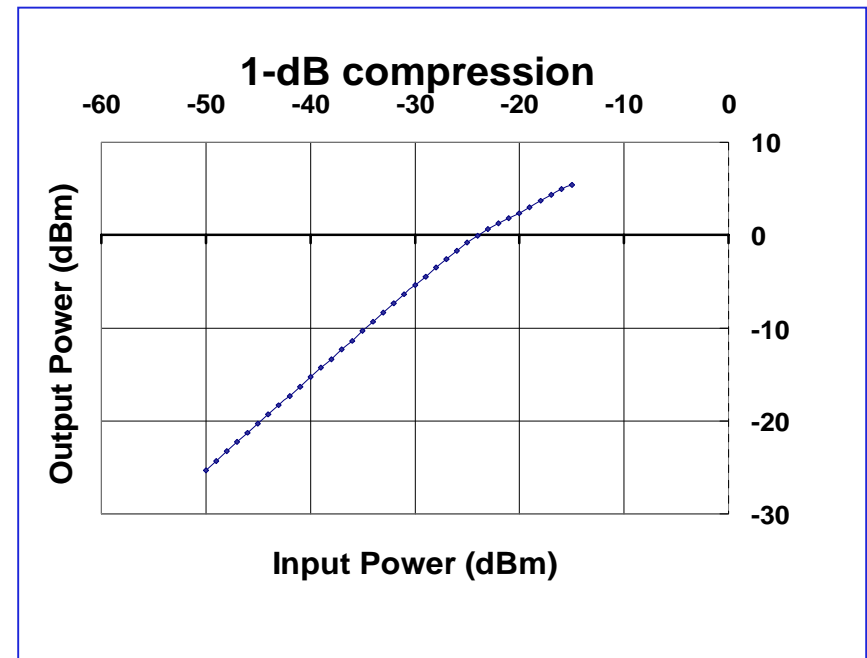LNA input = -43dBVrms
 Mixer output = -17.85dBVrms




1-dB compression at -25dBm
 (effective power)

Noise Measurement for Front-end

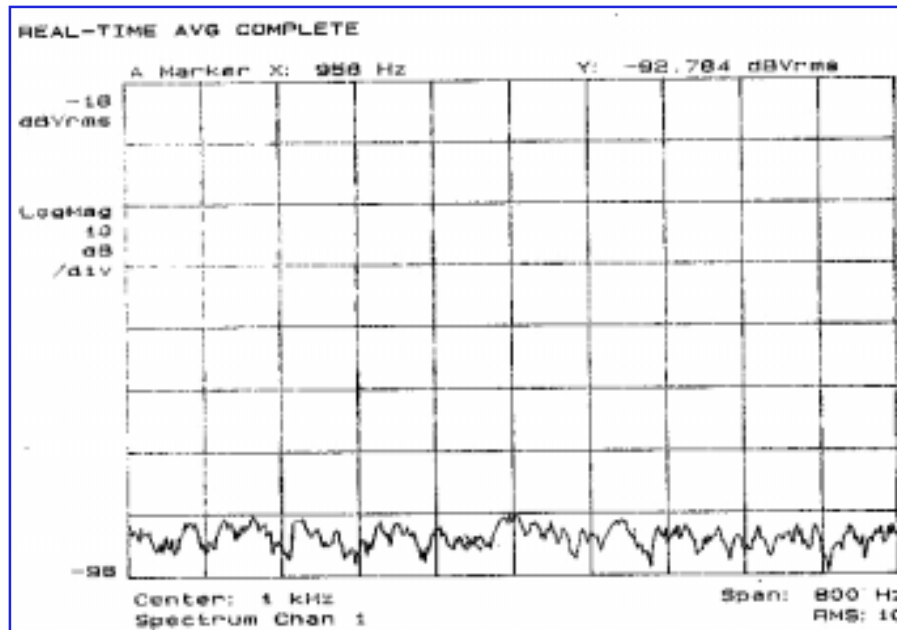

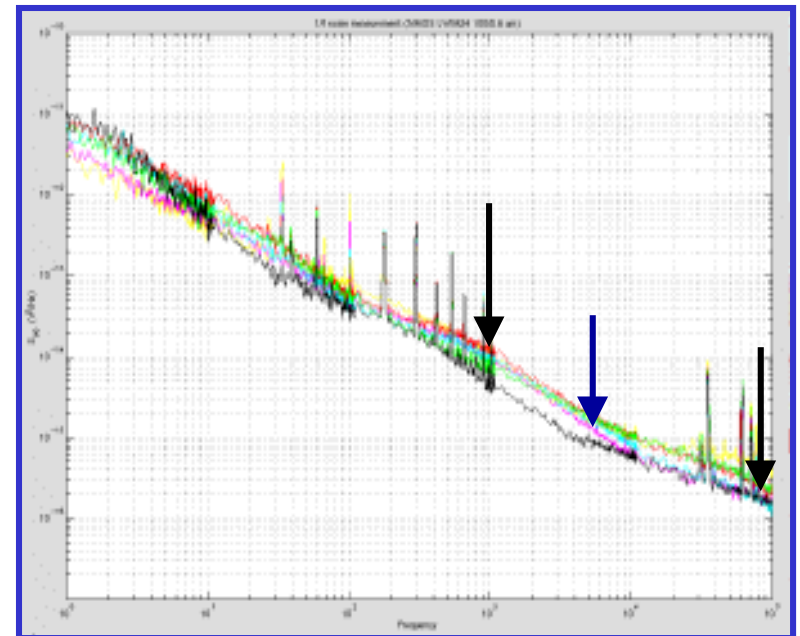This front-end:
 At 1KHz: $NF \approx 28\text{dB}$
 At 25KHz: $NF \approx 19.5\text{ dB}$







$1/f$ S_{VG} measurement
 (NMOS 100/0.6 μm)

WINS Integration

- Low Temperature Co-fired Ceramic
- Scrantom Engineering
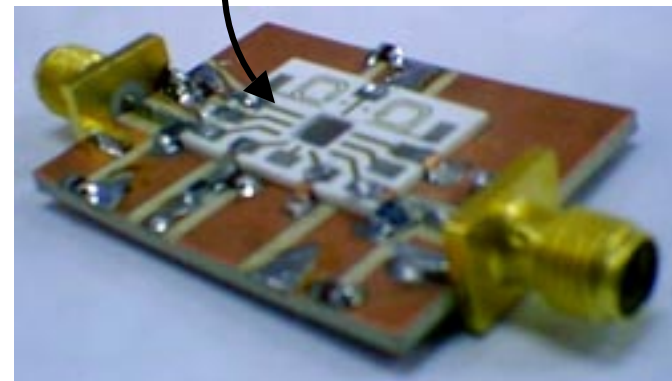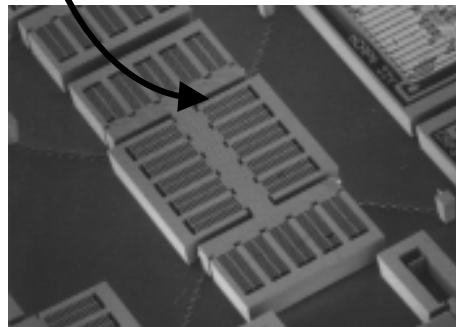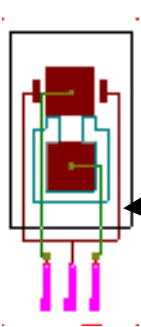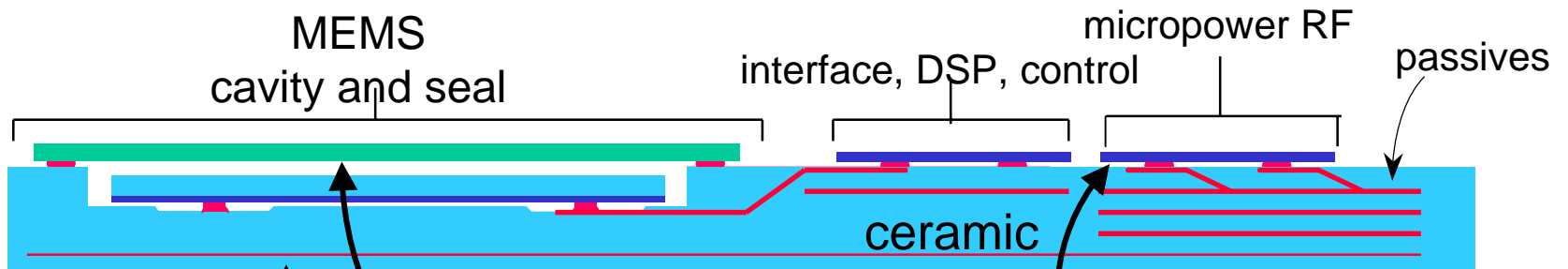
$$L = 20\text{nh} \quad Q \approx 20 \quad @ \quad 1\text{GHz}$$



Summary

- WINS project RF components trade off sensitivity for greatly reduced power consumption
- A front-end receiver with a total current consumption of $110\ \mu\text{A}$ has been developed and tested in $0.8\ \mu\text{m}$ CMOS technology
- The front-end includes a preselector which provides gain and filtering before the LNA
- The receiver has: Gain = 25dB, NF = 19.5dB, 1-dB compression = -25dBm,

Acknowledgment

- DARPA
- Scrantom Engineering, Inc. (SEI)
- Ms. M.Rofougaran, Dr. D. Pelhke,